

# **Digital Logic Gates and Boolean Algebra**


## **Part 1**

# Introduction

- **Boolean Algebra: named after mathematician George Boole (1815-1864).**
  - Base 2 algebra
    - All variables hold the literal value **True (1)** or **False (0)**
- **A (5v) digital circuit can have one of two values:**
  - Signal between 0 and 0.8 volt: **0 value**
  - Signal between 2 and 5 volts: **1 value**
    - Signal between 0.8 and 2 volts:
      - **undefined**, gate has no deterministic output.
- **Gates calculate various functions of one or more input values to generate an output.**
  - NOT, AND, OR, XOR, etc.
- **Computers are made up of gates.**
  - Performs all logical operations
  - Composed of connected transistors, resistors, capacitors, etc.
    - Digital circuits
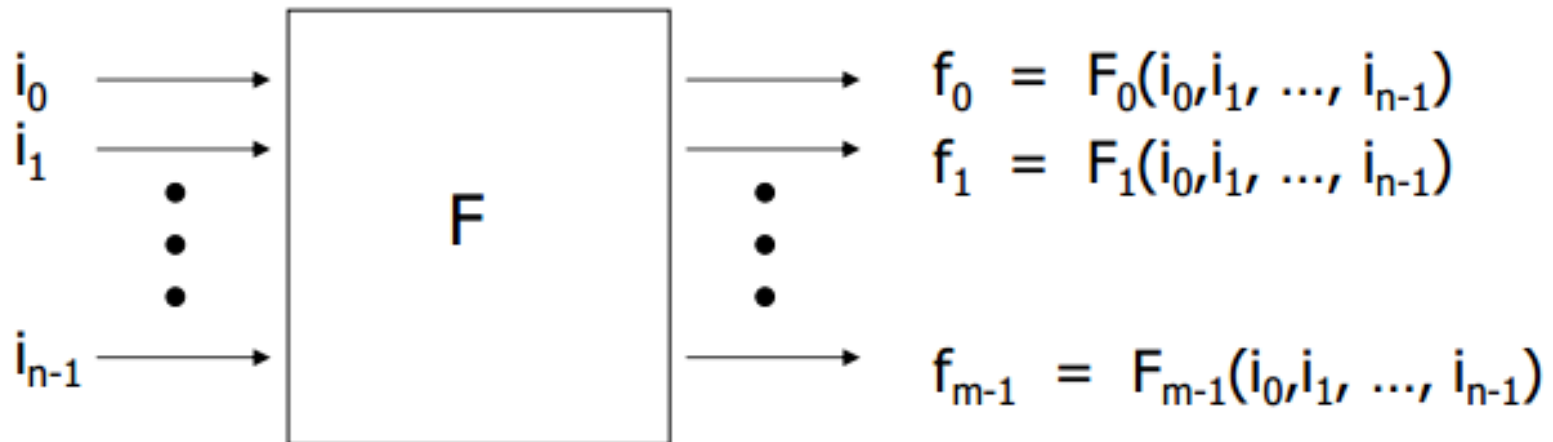
# Combinational Logic

- Translates a set of  $N$  input variables (0 or 1) by a mapping function.
- Uses Boolean operations to produce a set of  $M$  output variables (0 or 1).




# Boolean Operators

- **Basic Operators**
  - AND
  - OR
  - NOT
- **Other Useful Operators**
  - NAND
  - NOR
  - XOR
  - XNOR
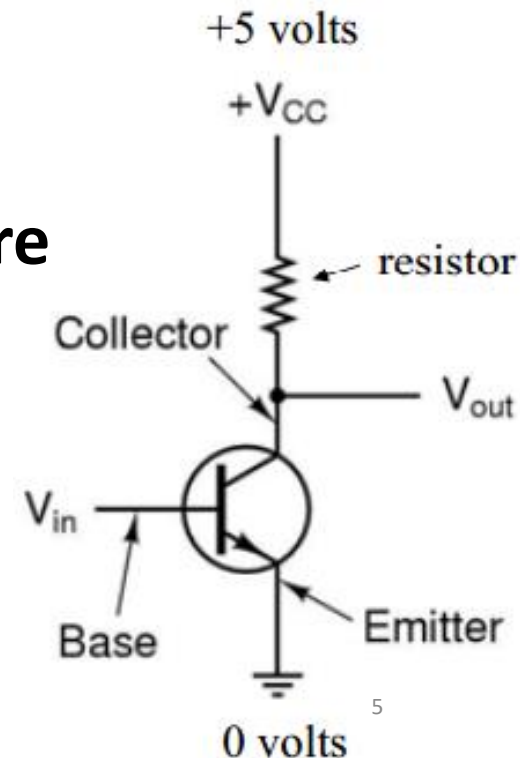
# NOT Operator (Inverter)

- 1 goes in, 0 comes out and vice versa
- Circuit:
  - When input ( $V_{in}$ ) is low, transistor turns off (infinite resistance) which means output is  $V_{cc}$ 
    - (0 in = 1 out)
  - When  $V_{in}$  is high, transistor acts like a wire to ground making  $V_{cc}$  0 volts.
    - (1 in = 0 out)
- Instant switching of states?
  - Takes a few nanoseconds.




# NOT Operator (Inverter)

- NOT truth table:

$X$	$\overline{X}$
0	1
1	0

- NOT gate symbol

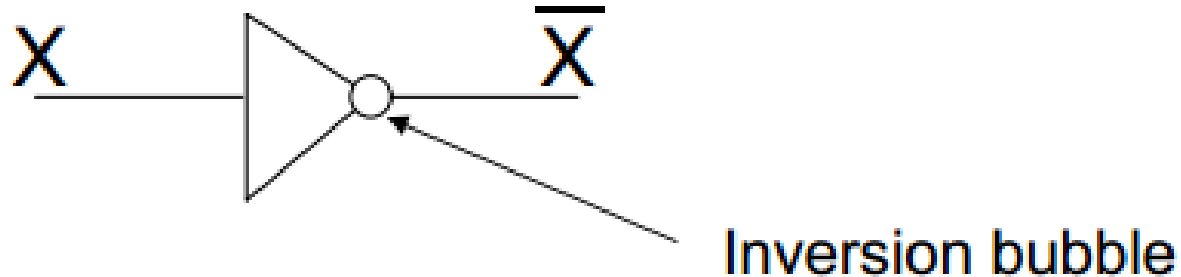


# AND Operator

- **AND truth table:**
  - Output is High if all inputs are high.
  - Otherwise, output is low.

A	B	$A \wedge B$
0	0	0
0	1	0
1	0	0
1	1	1

- **AND gate symbol**

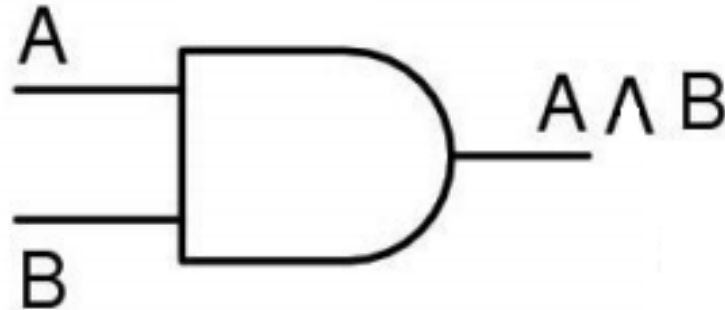


# NAND Operator

- **NAND truth table:**
  - Output is Low if all inputs are high.
  - Otherwise, output is high.

<i><b>A</b></i>	<i><b>B</b></i>	<i><b><math>\overline{A \wedge B}</math></b></i>
<b>0</b>	<b>0</b>	<b>1</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>

- **NAND gate symbol**

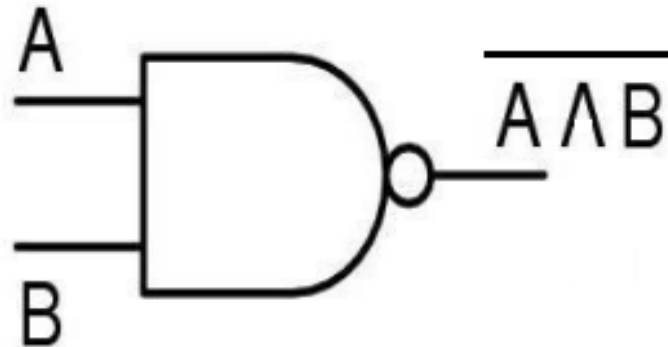



# NAND Operator


- **Simplified Circuit:**

- If  $V_1$  and  $V_2$  are both high, both transistors will conduct and produce a path to ground.

- $V_{out}$  will be low (0).

- If either  $V_1$  or  $V_2$ , or both, are low, the corresponding transistor resists, not allowing electricity to ground.

- $V_{out}$  will be high (1).

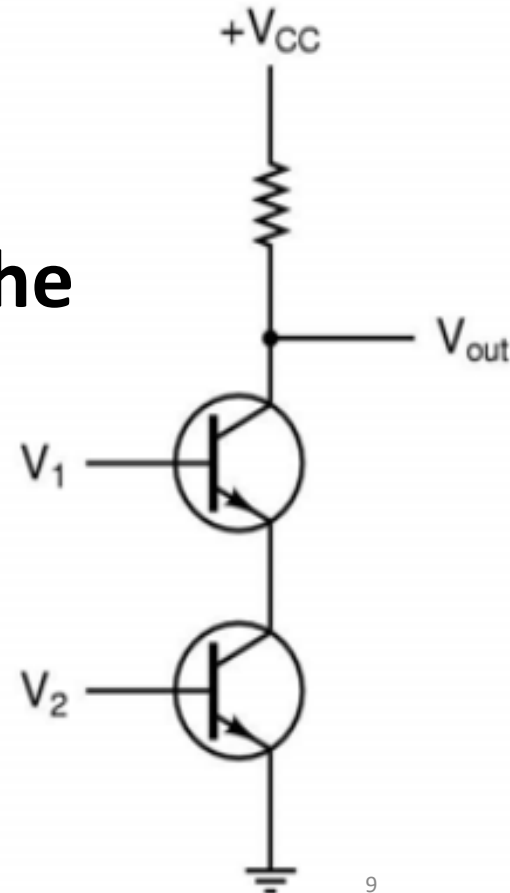


# OR Operator

- **OR truth table:**
  - Output is low if all inputs are low.
  - Otherwise, output is high.

<i><b>A</b></i>	<i><b>B</b></i>	<i><b>A ∨ B</b></i>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>

- **OR gate symbol**

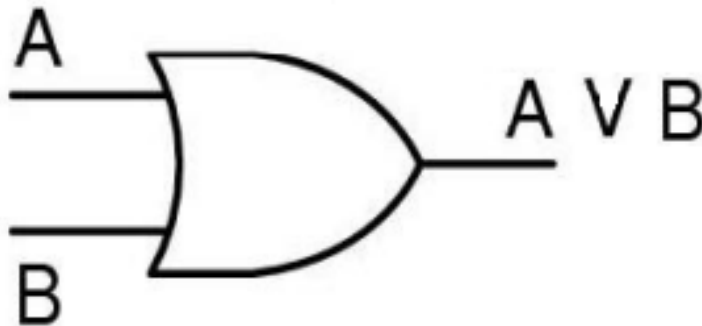


# NOR Operator

- **NOR truth table:**

- Output is High if all inputs are low.
- Otherwise, output is low.


<i><b>A</b></i>	<i><b>B</b></i>	<i><b><math>\overline{A \vee B}</math></b></i>
<b>0</b>	<b>0</b>	<b>1</b>
<b>0</b>	<b>1</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>0</b>

- **NOR gate symbol**

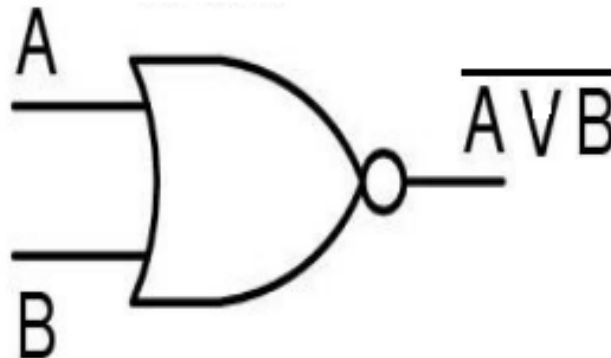
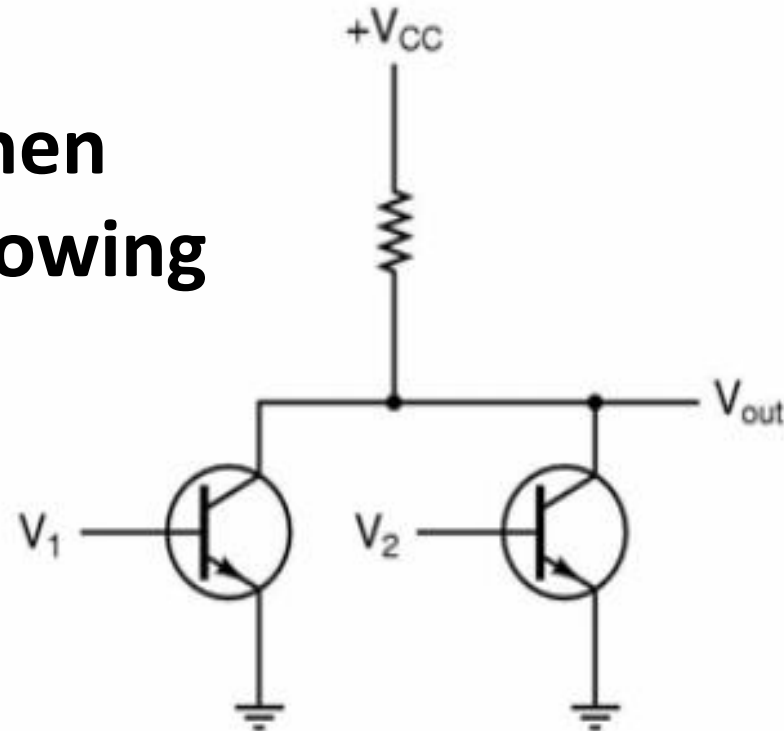
# NOR Operator

- **Simplified Circuit:**
  - If either  $V_1$  or  $V_2$ , or both, are high, then transistor will conduct and produce a path to ground.  
 $V_{out}$  will be low (0).
  - If both  $V_1$  and  $V_2$ , are low, then both transistors resist, not allowing electricity to ground.  
 $V_{out}$  will be high (1).




# XOR Operator

- **Exclusive-OR truth table:**
  - Output is High if all inputs are mismatched.
  - Otherwise, output is low.
- $XOR = A \oplus B = \bar{A}B + A\bar{B}$ 
  - Build this using AND, OR Gates?

<i>A</i>	<i>B</i>	<i>A</i> $\oplus$ <i>B</i>
0	0	0
0	1	1
1	0	1
1	1	0

- **XOR gate symbol**

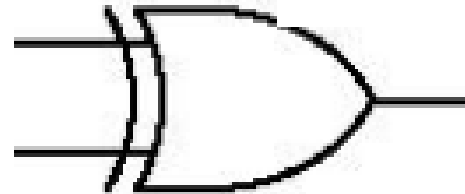

# XNOR Operator

- **Exclusive-NOR truth table:**


- Output is low if all inputs are mismatched.
- Otherwise, output is high.

<i>A</i>	<i>B</i>	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

- $XNOR = A \oplus B = AB + \overline{A}\overline{B}$

- Build this using AND, OR Gates?

- **XNOR gate symbol**

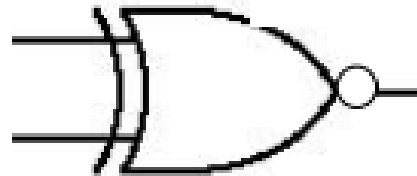


# Three Input AND Gate



A	B	C	$A \wedge B \wedge C$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

# Three Input Or Gate

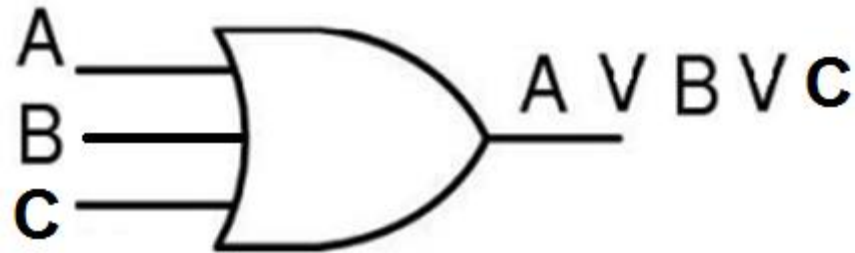

<b>A</b>	<b>B</b>	<b>C</b>	<b><i>A V B V C</i></b>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1